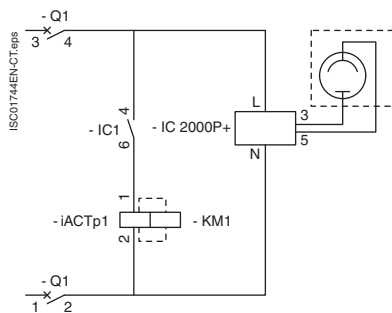


Anti-interference protection for sensitive devices

How to prevent brief voltage surges from going through the cables and disturbing sensitive devices?

- The iACTp auxiliary, snapped onto the left-hand side of the iCT contactor, filters conducted interference.
- The IC 2000P+ twilight switch with integrated time switch is also protected.

Control circuit



Power circuit



Products used	Qty.	Part no.
2P iC60N	1	
2P iCT	1	
iACTp	1	A9C15920
IC 2000P+	1	15483

